

Assignment - 7

$$I_{CMR} = 0.3 - 0.8$$

$$SR \geq 10V/\mu s$$

$$\text{Output swing} > 1V \quad G + 1 \cdot S = \left(\frac{\omega}{L}\right)$$

$$\text{Power} < 1mW$$

$$C_L = 1PF \quad V_{DD} = 10V \quad G_B W > 10M \Omega \quad 2Bv + 22V \quad 50.5mV \quad \text{QH}$$

$$m_{COX} = 300 \mu m \quad \mu_{COX} = 65 \mu m$$

$$L = 0.54 \mu m$$

$$10V - 2Bv =$$

$$V_{DD} = 7V - 22V$$

$$C_C \geq 0.22 C_L \Rightarrow C_C \geq 0.22(1PF) \Rightarrow C_C \geq 0.22 \text{ pF}$$

$$[C_C = 2 \text{ pF}]$$

$$\Rightarrow SR > 10V/\mu s \Rightarrow I_{SS} > (2 \text{ pF})(10V/\mu s)$$

$$(9TV + 2V) > 2Bv \Rightarrow I_{SS} > 20 \text{ mA}$$

For MOSFET

we use $G_B W$ to find g_m , minimum

$$\frac{g_m}{C_C} = G_B W = 2\pi \times 10 \times 10^6 \Rightarrow g_m = 2\pi \times 10^7 \times 20 \times 10^{-6}$$

$$\frac{(9TV) - 2Bv}{+0.2} = \frac{40\pi \times 10 \times 10^{-12}}{400\pi \times 10^{-12}}$$

$$= \frac{-10}{-4\pi \times 10}$$

$$= 1.28 \times 10^{-4}$$

$$= 125.663 \text{ A/m}$$

$$\left(\frac{\omega}{L}\right)_1 = \frac{g_m^2}{2\left(\frac{I_{SS}}{2}\right) (\mu_P C_{ox})} = \frac{(125 \cdot 663 \times 10^{-6})^2}{(20 \times 10^{-6})(65 \times 10^{-6})}$$

$$\left(\frac{\omega}{L}\right)_1 = 12.142 \quad \left(\frac{\omega}{L}\right)_2$$

$$\Rightarrow V_{in \text{ min}} \Rightarrow V_{SS} + V_{gs3} + V_{sg3} + V_{DT} = 0 + V_{gs3} + (N_{VT} + V_{DT}) + V_{DT}$$

$$V_{SG} - V_T = V_{DN}$$

$$= V_{gs3} - V_{Th}$$

$$\text{For MOSFET } 1 \Rightarrow V_{sd1} > V_{sg1} - |V_{TP}|$$

$$-V_d \Rightarrow V_{sg1}$$

$$\text{For MOSFET } 1 \Rightarrow V_{sd1} > V_{sg1} - |V_{TP}|$$

From ΔCMR minimum $V_d < V_g + |V_{TP}|$
we will find

$$\left(\frac{\omega}{L}\right)_{3,4}$$

$$V_g > V_{d1} - |V_{TP}|,$$

minimum gate voltage

$$V_g > V_{gs3} - |V_{TP}|,$$

$$\frac{0.3}{2 \times 10^{-6} \times 10^{-6}} = V_{gs3} - (V_{TP}),_{sat}$$

$$238200.281 =$$

Threshold voltage assume 0.4V

$$V_{DD} - V_{TH} = 8 - 0.4 = 7.6V$$

$$0.3 = \sqrt{g_{SD}} - 0.4V \Rightarrow \boxed{\sqrt{g_{SD}} = 0.7V}$$

$$2 \times 10^{-6} = 0.7^2 \text{ mV}$$

$$I_{D3} = \frac{\mu_n C_O}{2} \left(\frac{w}{l}\right)_3 (0.75 - 0.4V)$$

$\Rightarrow \left(\frac{w}{l}\right)_3 = 0.74$ (calculated)

$$\left(\frac{w}{l}\right)_3 = \frac{1.0 \times 10^{-6} \times 2}{3.00 \times 10^{-6} \times 0.3} = 0.74$$

$$\left(\frac{w}{l}\right)_3 = \left(\frac{w}{l}\right)_4 = 0.74$$

$$1.01 \cdot 0.74 = 0.74 \left(\frac{w}{l}\right)$$

\Rightarrow From ICMP maximum current with Freq 100Hz

$$\frac{1}{2} \left(\frac{w}{l}\right)_{5,6} I_{DS(on)}$$

\Rightarrow I am assuming MOSFET 5 and 6 are same

$$V_{IN(max)} = V_{DD} - V_{DS(on)} - V_{DS(on)} - V_{SG1}$$

$$\sqrt{V_{DS(on)}} = \sqrt{V_{DS(on)}}$$

$$V_{SG1} = \sqrt{\frac{2(1.0 \times 10^{-6})}{6.5 \times 10^{-6} \times (12.147)}} \text{ since } S = 0.4V$$

$$\boxed{V_{SG1} = 0.609}$$

$$\left(\frac{w}{l}\right)_{5,6} \cdot \frac{2mB}{C} = 2mB$$

$$V_{IO} = 0.8 = 1.8 - 2V_{OV} - 0.609$$

$$2V_{OV} = \Sigma B^V \quad \Sigma V_{OV} = \Sigma B^V = 2.0$$

$$V_{OV\ 5,6} = 0.1955$$

$$\Rightarrow \text{calculating } \left(\frac{\omega}{\tau}\right)_{S,6}$$

$$20 \times 10^{-6} = \frac{1}{2} (55 \times 10^{-6}) \left(\frac{\omega}{\tau}\right)_{S,6} (0.1955)^2$$

$$\left(\frac{\omega}{\tau}\right)_{S,6} = 16.101$$

$$+f_0 = +\left(\frac{\omega}{\tau}\right) = \left(\frac{\omega}{\tau}\right)$$

\Rightarrow unity gain freq (ω_{UB})

$$\text{unity} = \frac{g_m}{C_C}$$

$$\text{second pole} = \frac{g_m}{C_L}$$

The phase margin is optimized $\omega_{UB} = 210V$

$$\omega_{P2} = 3.2 \omega_{UB}$$

$$\frac{g_m}{C_L} = 3.2 \frac{g_m}{C_C}$$

$$\Rightarrow g_m = 3.2 g_m \left(\frac{C_L}{C_C}\right)$$

$$\Rightarrow g_{m8} = (2 \cdot 2) \left(\sqrt{2 \cdot I_d (300 \times 10^6)} (0.74) \right) \left(\frac{1}{2} \right)$$

$$(418.0) \left(\frac{1}{2} (3 \cdot 2) \right) \left(\frac{1}{2} \right) \left(\frac{1}{2} \right) \times 0.74 = 87$$

$$g_{m8} = 0.00007329 = 87$$

$$g_{m8} = 73.29 \mu s$$

$$AN800-01 = 87$$

$$\Rightarrow \left(\frac{\omega}{L}\right)_8 = \frac{g_{m8}^2}{(2I_d)(n_{ox})}$$

~~we don't know I_{ds8}~~

so we should use some other method

||

For MOSFET 4 \leftrightarrow 8

Some vdsat

$$\frac{g_{m4}}{g_{m8}} = \frac{(V_c)_4}{\left(\frac{\omega}{L}\right)_8} = \frac{0.74}{\left(\frac{\omega}{L}\right)_8} = \frac{66.633 \mu s}{73.29}$$

$$V_{Dsat} = 24.0 - 2BV - 2V$$

$$= 24.0 - \frac{0.74}{\left(\frac{\omega}{L}\right)_8} = 0.909$$

$$\Rightarrow \left(\frac{\omega}{L}\right)_8 = 0.814$$

$$I_8 = \frac{(gma_8)^2 (d_{81} \times 0.8) (b=8)}{2 \mu n \cos\left(\frac{\pi}{2}\right) (8)} = \frac{(73.29 \times 10^{-6})^2}{2 (300 \times 10^{-6}) (0.814)}$$

$$I_8 = 0.00001099 \text{ A} = 8 \text{ mA}$$

$$(I_8 = 10.998 \text{ mA})$$

$$2 \text{ N.P.S.E.F} = 8 \text{ mA}$$

For MOSFET 7

$$\frac{(\omega_L)}{I_7} = \frac{8bI}{(x_0)n^A(b=8)} = \frac{8(0.998 \times 10^{-6})}{20 \times 10^{-6}} = 0.399 \text{ A/m}$$

$$\left(\frac{\omega}{L}\right)_7 = 8.853$$

M₅ & M₆ (Blasting)

$$M_{5,6} \Rightarrow V_{sg} - V_{th5} = \frac{V_{dd} - V_{th5}}{8\left(\frac{\omega}{L}\right)} = 0.195 \text{ V}$$

$$V_s - V_{g5} - 0.45 = 0.195 \text{ V}$$


$$V_g = 1.8 - 0.45 - 0.195 \text{ V}$$

$$V_{g5} = 1.1545 \text{ V}$$

$$V_{g6} = V_{D6} - V_{Th} \quad (\text{at } mB = nA) \quad (\approx 0.308)$$

$$0.1955 = (1.8 - 0.1985) - V_{g6} - 0.45$$

$$V_{g6} = (0.959)V$$

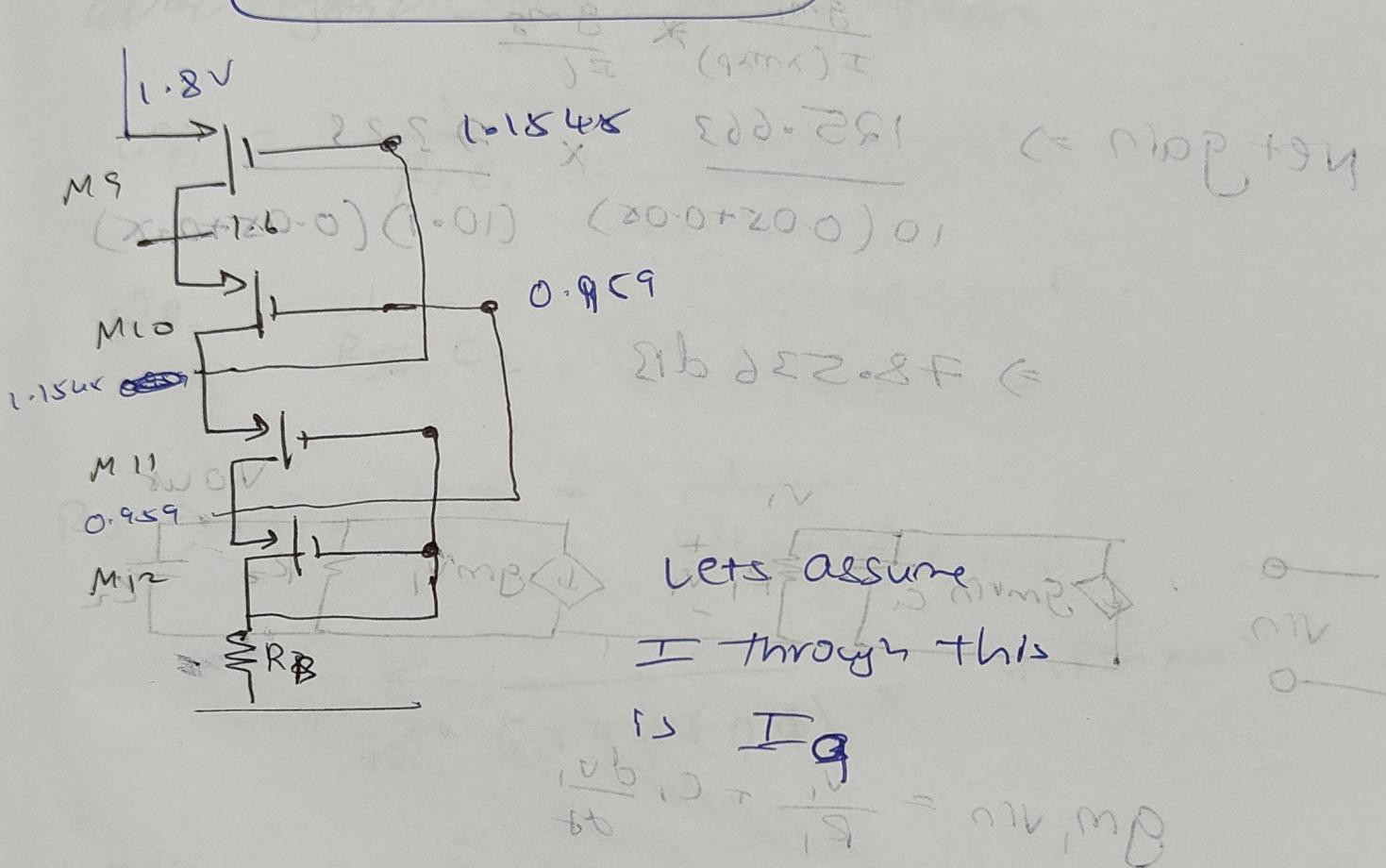

$$\Rightarrow \text{Power consumption}$$





$$= (I_Q + 20 \times 10^{-6} + 10.998 \times 10^{-6}) (1.8)$$

$$= 55.796 \mu W + (I_S)(1.8)$$

$$I_Q(1.8) + 55.796 \mu W \leq 1000 \mu W$$

$$I_Q(1.8) \leq 994.204 \mu W$$

$$I_Q \leq 524.557 \mu W$$

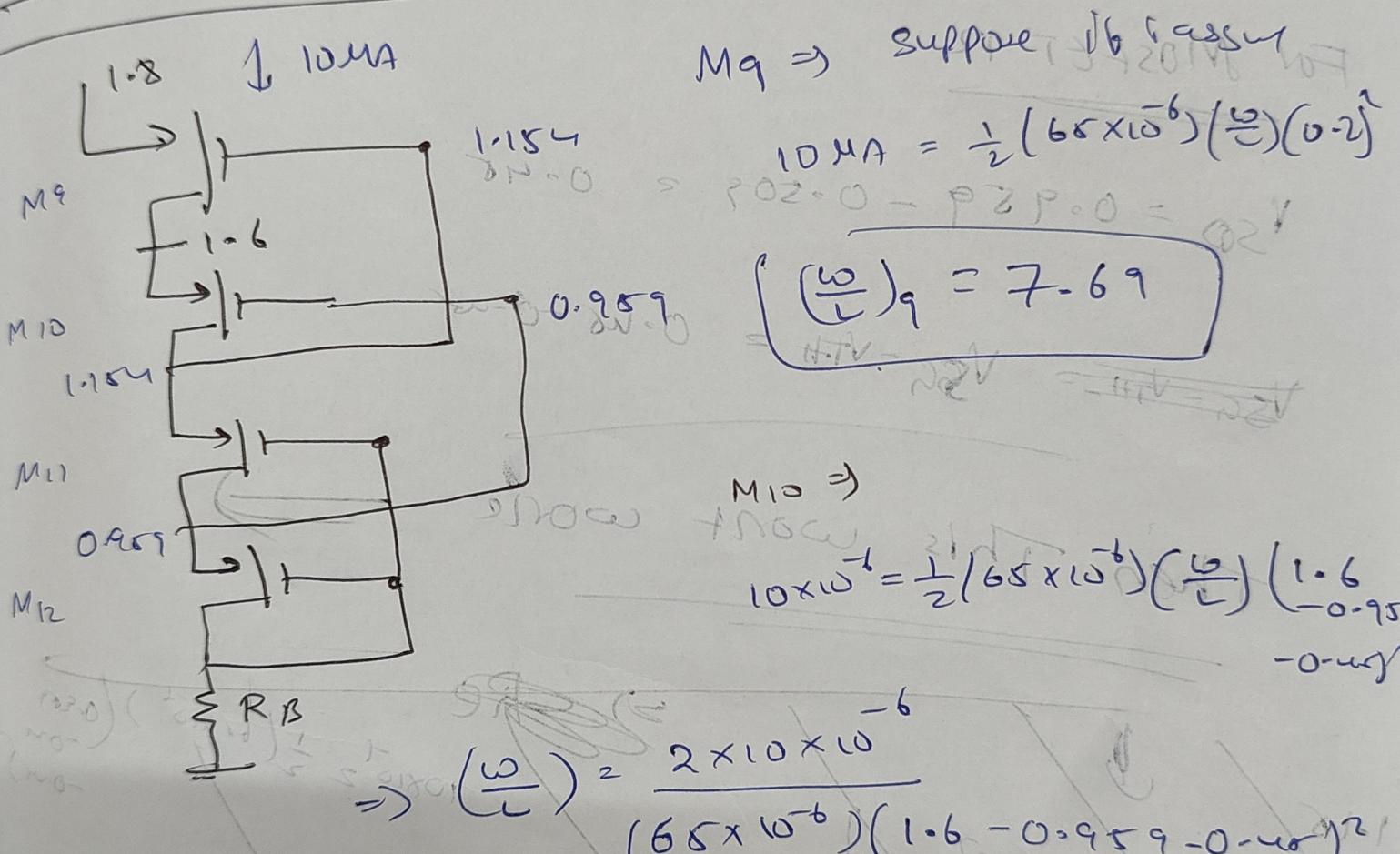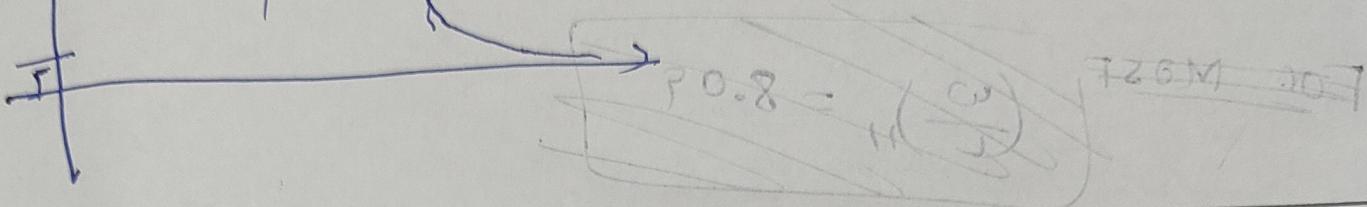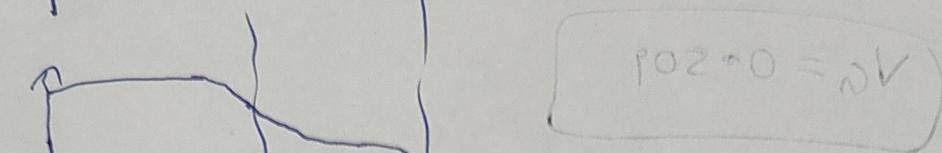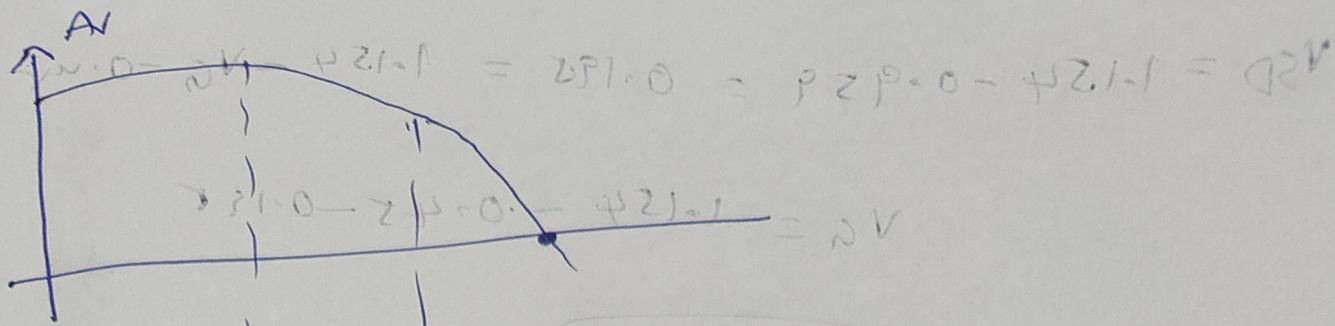

For MOSFET 1)

$$V_{SD} = 1.154 - 0.959 = 0.195 = 1.154 - V_G - 0.45$$

$$V_G = 1.154 - 0.45 - 0.195$$

$$(V_G = 0.509)$$

For MOSF

$$\left(\frac{d}{L} \right)_H = 8.09$$


For MOSFET 2)

$$(5.0)(0.01 \times 20) \frac{1}{L} = AM_01$$


$$V_{SD} = 0.959 - 0.509 = 0.45$$

$$V_{SG} - V_{TH} = V_{SG} - V_{TH} = 0.45 + 0.45$$

$$AM_01 \downarrow 8.09$$

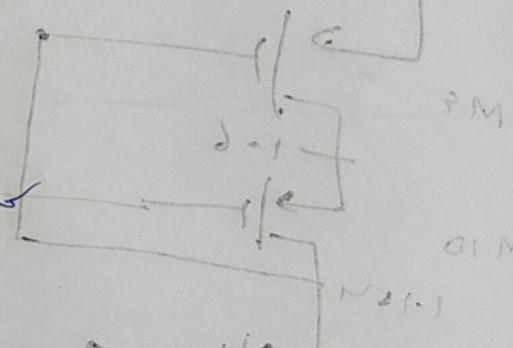

Then This wont work

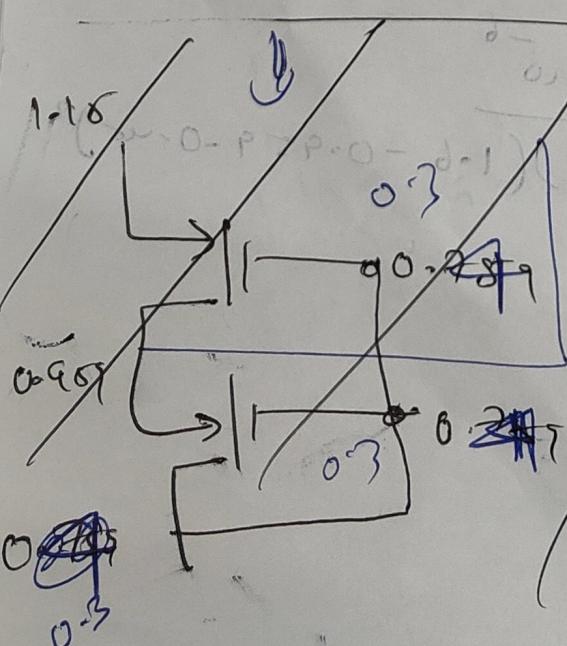


Revised Values

$$8.8 = \left(\frac{d}{L} \right)$$

$$10 \times 10^{-6} = \frac{1}{2} (65 \times 10^6) \left(\frac{d}{L} \right)_H (0.45 - 0.389 - 0.45)$$

Revised

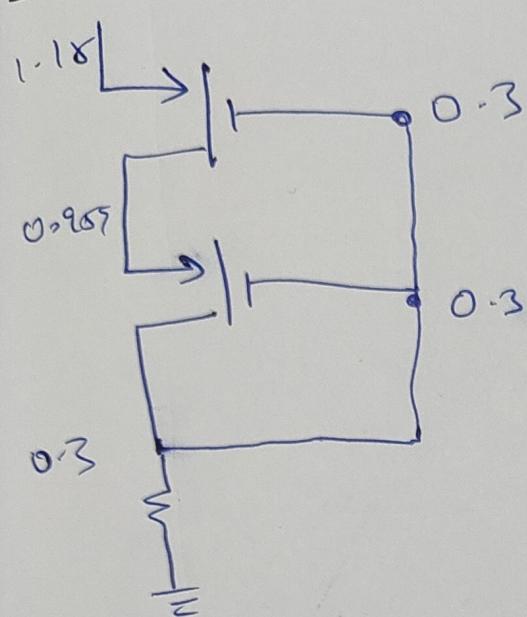

$$M_{11} \Rightarrow \left(\frac{\omega}{\nu}\right)_{11} = \frac{2 \times 10 \times 10^6}{(1.18 - 0.3 - 0.959)}$$

$$\left(\frac{\omega}{\nu}\right)_{11} = 1.92$$

$$M_{12} \Rightarrow \left(\frac{\omega}{\nu}\right)_{12} = \frac{2 \times 10 \times 10^6}{65 \times 10^6}$$

(0.959 - 0.3 - 0.3)


$$\left(\frac{\omega}{\nu}\right)_{12} = 7.69$$

$$\underline{\text{Gain}} \Rightarrow A_v = -g_{m1} \left(\frac{R_2}{R_1} \right) \frac{V_{in} - V_{out}}{2V} = \frac{-g_{m1}}{2V} = \underline{-g_{m1}}$$

$\frac{g_{m1}}{I(\lambda m_p)} * \frac{g_{m2}}{I(\lambda m_p)}$

Net gain $\Rightarrow \frac{125.663}{10(0.05+0.05)} \times \frac{23.28}{(10.1)(0.05+0.05)}$

$\Rightarrow 78.536 \text{ dB}$

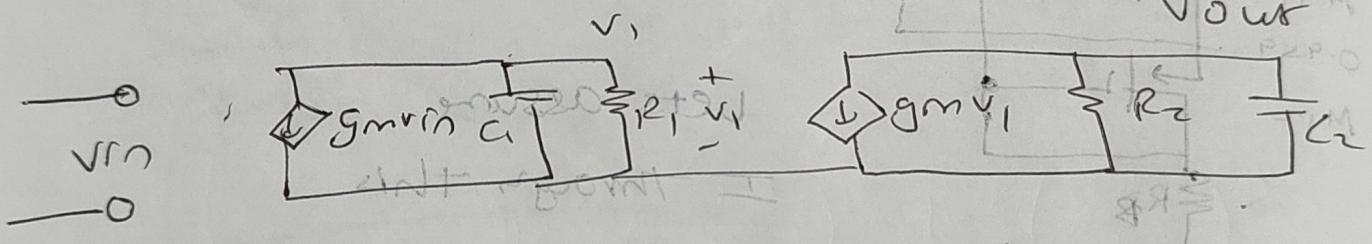

$$g_{m1} v_{in} = \frac{v_1}{R_1} + C_1 \frac{d v_1}{dt}$$

$$(8.1) \quad v_1 = g_{m1} v_{in} \left(\frac{R_2}{1 + S R_1 C_1} \right)$$

$$\Rightarrow (8.1) g_{m2} v_1 + \frac{v_{out}}{R_2} = C_2 \frac{d v_{out}}{dt}$$

$$v_{out} = g_{m2} v_1 \left(\frac{R_2}{1 + S R_2 C_2} \right) \quad (8.1) p^T$$

$$v_{out} = g_{m1} g_{m2} R_1 R_2 \frac{v_{in}}{(1 + S R_1 C_1)(1 + S R_2 C_2)} \quad (8.1) p^T$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = \frac{g_{m1} g_{m2} R_1 R_2}{(1 + S R_1 C_1)(1 + S R_2 C_2)}$$

$$\omega_{P_1} = \frac{1}{2\pi R_1 C_1} = \frac{1}{(5 \times 10^6)(0.05 + 0.05)} = 5 \text{ rad/s}$$

$$R_1 = 20 \Omega / 100 \Omega = \frac{1}{(10 \times 10^6)(0.05 + 0.05)} = 10^6 \Omega$$

~~Wavelengths of oscillations~~ = ω_{D1}

$$\omega_{P_1} = \frac{1}{R_1 C_1} \quad \text{Ansatz}$$

$$\omega_{P_2} = \frac{1}{R_2 C_2} = \frac{1}{8 \times 10^6 \times 10^{-12}} = 8 \times 10^{12} \text{ rad/s}$$

$$R_2 = 20 \Omega / 100 \Omega = \frac{1}{gds_7 + gds_8} = \frac{1}{9.17 \times 10^{-6} \times (0.9) \times (0.01)} = 1.17 \times 10^6 \Omega$$

C_1 would be $(10^{-12} \text{ F}) \times 10^{-12} = 10^{-24} \text{ F}$ = 10^{-24} Farad

Let's assume 15 fF

C_2 is $C_2 = 1 \text{ PF}$

$$\omega_{P_1} = \frac{1}{2\pi (10^6) (15 \times 10^{-12})} = \frac{6.67 \times 10^7}{2\pi} \text{ rad/s}$$

$$= 10610329.54 \text{ rad/s}$$

$$= 10.61 \times 10^6 \text{ Hz}$$

$$\omega_{P2} = \frac{1}{2\pi(9.12 \times 10^8)(10^{-12})} = 17.35 \times 10^4 \text{ Hz}$$

$$GBW = (78.536 \text{ dB})(17.35 \times 10^4)$$

~~degam~~

~~dominant pole~~

$$= 1465883577 \text{ Hz}$$

$$= 14.65 \times 10^8 = 1.465 \text{ GHz}$$

~~phase margin~~

$$ZH(s) = -\tan^{-1}\left(\frac{\omega}{\omega_{P1}}\right) - \tan^{-1}\left(\frac{\omega}{\omega_{P2}}\right)$$

$$PM = 180^\circ - \tan^{-1}\left(\frac{1.465 \times 10^8}{10.61 \times 10^6}\right) - \tan^{-1}\left(\frac{1.465 \times 10^8}{17.35 \times 10^4}\right)$$


$$PM = 0.421^\circ$$

$$\frac{F_{01 \times 0.0}}{D_2} = \frac{1}{(2\pi 61 \times 21)(201) \pi \delta} = 1 \text{ gW}$$

at $\omega = 10^8 \text{ rad/s}$

$$= 10^8 \text{ rad/s}$$

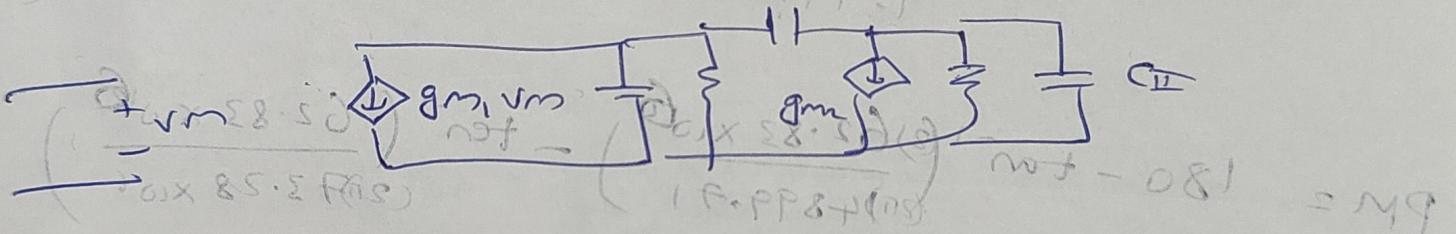With compensation capacitor
 $100 \times 3128.58 = 31285.8$ pF



$$w_p = \frac{(\lambda_n + \lambda_p) I_2 - (\lambda_n + \lambda_p) I_8}{g_m g_c}$$

$$w_{P_2} = \frac{g_m z}{C_2}$$

$$w_f = \frac{g m_2}{C c}$$

$$w_{P_1} = \frac{(0.4) (10 \times 10^6) (0.1) (10.92 \times 10^6)}{(73.29 \times 10^{-6}) (2 \times 10^{-14})}$$

$$= \frac{14899.071}{2} \text{ rad/sec} \leq 7.449 \times 10^3 \frac{\text{rad}}{\text{sec}}$$

$$\omega_1 = \frac{g m_8}{c c} = \frac{73.28 \times 10^6}{2 \times 10^{-12}} = \frac{73.28 \times 10^6 \text{ rad}}{2 \text{ sec}}$$

$$= 36.64 \times 10^6 \text{ rad/sec}$$

$$\omega P_2 = -\frac{g m_8}{c L}$$

$$= \frac{73.28 \times 10^6}{10^{-12}} = 73.28 \times 10^6 \text{ rad/sec}$$

$$GBW = \frac{g m_1}{2 \pi c c} = \frac{125.663 \times 10^6}{2 \times 10^{-12}}$$

$$9.99 \text{ MHz} = 62.8315 \times 10^6 \text{ rad/sec}$$

$$PM = 180 - \tan^{-1} \left(\frac{(2) 62.83 \times 10^6}{(2) 36.64 \times 10^6} \right) - \tan^{-1} \left(\frac{62.83 \times 10^6}{36.64 \times 10^6} \right)$$

$$\frac{8I(96+8)}{22.8 \text{ mB}} = -\tan^{-1} \left(\frac{62.83 \times 10^6}{36.64 \times 10^6} \right)$$

$$\frac{mB}{50} = 59.6$$

$$\boxed{PM = 66.9642}$$


$$\boxed{PM = 67.029}$$

$$\frac{mB}{50} = 59.6$$

$$\frac{(1.01s)(0.99 \times 10^6)(1.0)}{(1.01s)(0.99 \times 10^6)(1.0)} = 1.96$$


$$E_{\text{exp-ppf}} = 307.608 \text{ if } 0.998 + 1 =$$

~~With Compens~~

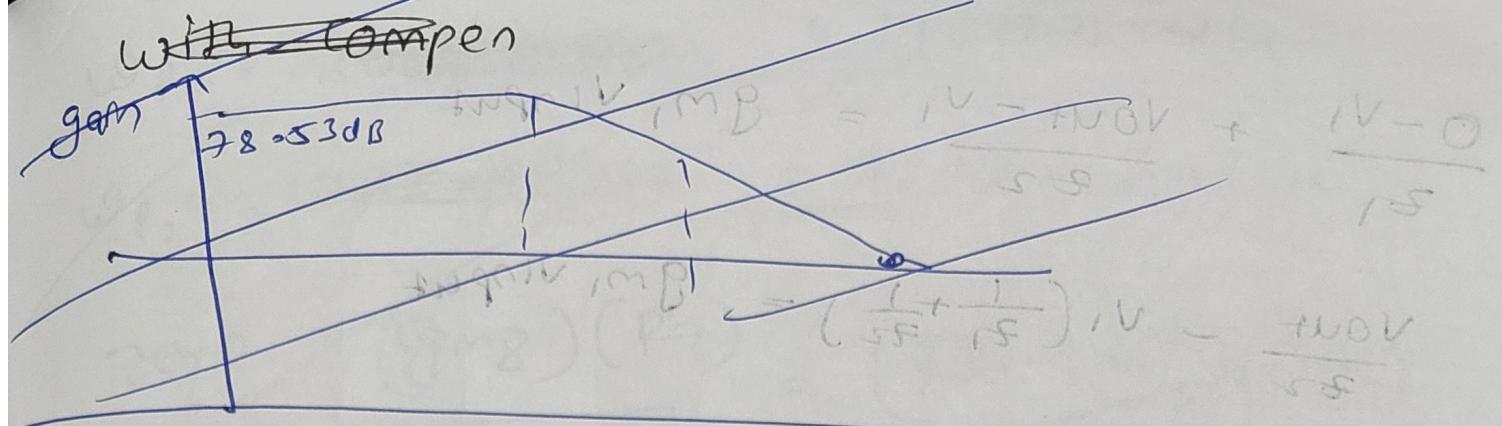

~~Compensation + Resistor~~
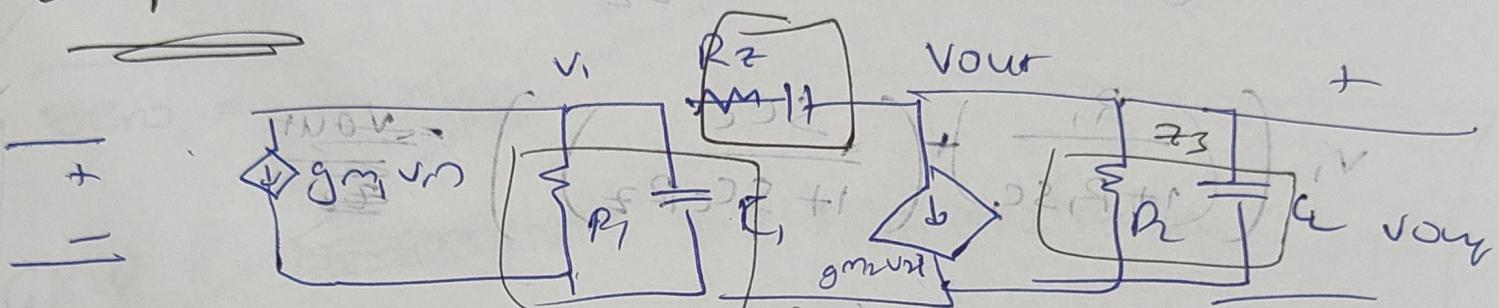
$$z_2 \left(\frac{1}{55} + \frac{1}{18} \right) V$$



$$100V_{1MB} \rightarrow \left(\frac{z_2}{z_1} \right) + 100 =$$

$$\frac{0 - V_1}{z_1} + \frac{V_{out} - V_1}{z_2} = g_{m1} V_{in} \quad \text{--- (1)}$$

$$z_1 \Rightarrow \frac{1}{z_1} = \frac{1}{R_1} + SC_1 = \left(\frac{1 + R_1 S C_1}{R_1} \right) + 100$$

$$z_1 = \frac{R_1}{1 + R_1 C_1 S}$$

$$z_2 \Rightarrow R_2 + \frac{1}{S C_2} \quad \text{out} \quad \leftarrow \text{non in.}$$

$$z_3 \Rightarrow z_3 = \left(\frac{R_2}{1 + R_2 C_2 S} \right) \left(\frac{1 + R_1 S C_1}{R_1} \right)$$


$$\frac{V_1 - V_{out}}{z_2} + \frac{0 - V_{out}}{z_3} = -g_{m2} V_1 \quad \text{--- (2)}$$

$$(55)(8MB) V_1 \left(\frac{1}{z_2} - g_{m2} \right) = V_{out} \left(\frac{1}{z_2 R_2} + \frac{1}{z_3} \right)$$

$$\frac{0 - V_1}{Z_1} + \frac{V_{\text{out}} - V_1}{Z_2} = g_m V_{\text{input}}$$

$$\frac{V_{\text{out}}}{Z_2} - V_1 \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = g_m V_{\text{input}}$$
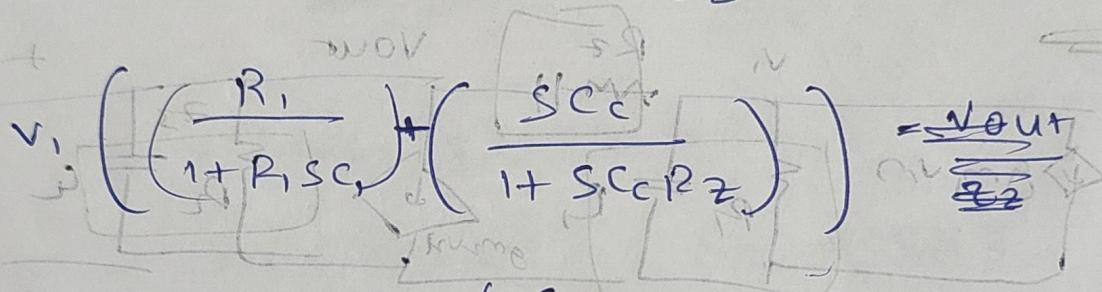
$$V_1 \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = \frac{V_{\text{out}} + g_m V_{\text{input}}}{Z_2}$$



$$= V_{\text{out}} \left(\frac{S_{\text{cc}}}{1 + S_{\text{cc}} R_2} \right) - g_m V_{\text{input}}$$

$$AV_{\text{MB}} = \frac{V - V_{\text{out}}}{V - 0}$$

$$\frac{V_{\text{out}} \left(\frac{1}{Z_2} + \frac{1}{Z_3} \right)}{\left(\frac{1}{Z_2} - g_m \right)} = \frac{R_1 + S_{\text{cc}} R_2 R_1 + S_{\text{cc}} + S^2 C_{\text{c}} R_1}{\left(\frac{1}{Z_2} - g_m \right)} = 1.5$$

$$\underline{\underline{\text{Finally} \Rightarrow A_{\text{DC}} \left(1 - \frac{s}{2} \frac{1}{Z_2} + \frac{s}{Z_2} \right)}} \\ \underline{\underline{\left(1 + \frac{s}{P_1} \right) \left(1 + \frac{s}{P_2} \right) = 3.5 \quad (= 3.5)}}$$

$$\omega_{P_1} \approx \frac{1}{R_1 C_1} = \frac{\omega_{P_3}}{2(V_0 - 0) + \frac{1}{R_2 C_2}}$$

but

$$\left(\frac{1}{2.5} \omega_{P_3} \right) \frac{1}{R_2 C_2} = \left(\frac{g_m}{Z_0} \right) \frac{(g_m)(R_2)}{C_2}$$

freq response without compensation

⇒ when the series resistance is connected

with Miller capacitor

⇒ The nulling resistor introduced a weak 3rd pole which pushes the Right

half plane zeros away from the system

$$P_3(\text{new}) = -Gm_8 \left(\frac{1}{C_C} + \frac{1}{C_1} + \frac{1}{C_L} \right) R_2$$

$$Z_1 = \frac{1}{\left(R_2 - \frac{1}{Gm_8} \right) C_C}$$

$$R_2 \geq \frac{1}{Gm_8} \quad \Rightarrow \quad \text{If this is not taken as it would lie in left}$$

half of s-plane providing phase lead instead of phase lag

⇒ This would result the total phase lag of 180° deg

⇒ Unstability

$$R_3 = \frac{1}{g m_8} = \frac{1}{73.28 \times 10^6} = 13.646 \times 10^3 \text{ N}$$

$$P_3^{\text{new}} = \frac{(73.28 \times 10^6)(13.646 \times 10^3)}{2 \times 10^{-12} + \frac{1}{1 \times 10^{12}} + \frac{1}{15 \times 10^{12}}} = 68.16 \times 10^{13} \text{ rad/sec} \approx 2164 \text{ rad/sec}$$

$$\text{PM} = 180 - \tan^{-1} \left(\frac{G B_{\text{ext}}}{\omega P_1} \right) - \tan^{-1} \left(\frac{G B_{\text{ext}}}{\omega P_2} \right) - \tan^{-1} \left(\frac{G B_{\text{ext}}}{\omega P_3} \right)$$

$$Z_1 =$$

$$M_{11} = N_{\text{PS}}^{\text{sat}} = V_{SA} - V_{TP}$$

$$N_{SD}^{\text{sat}} = V_{SA} - V_{TP}$$
~~$$0.959 - 0.154 = 0.805$$~~
~~$$0.959 - 0.154 = 0.805$$~~


$$1.154 - 0.959 = 0.195$$

$$1.18 - V_A = 0.2$$


$$V_A = 1.18 - 0.612 \text{ NT}$$

ANSWER


Bode Plot — Magnitude

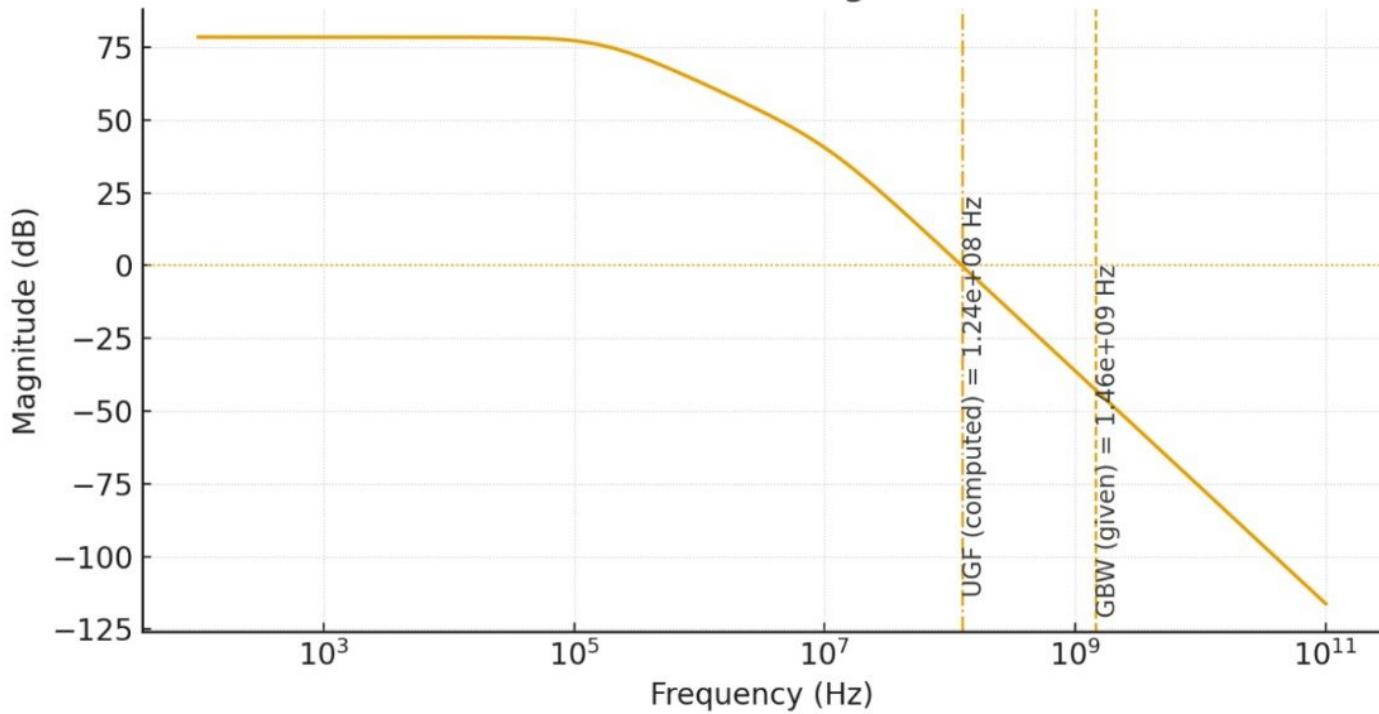

Bode Plot — Phase

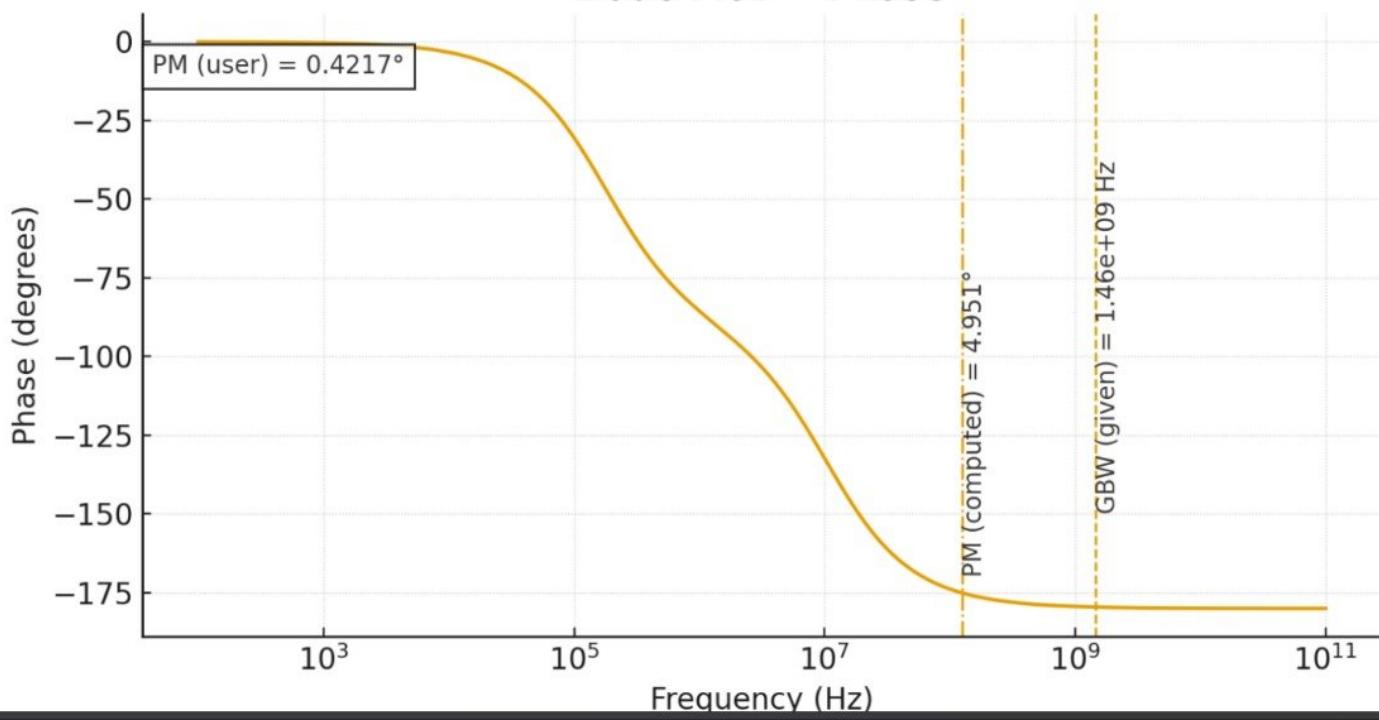

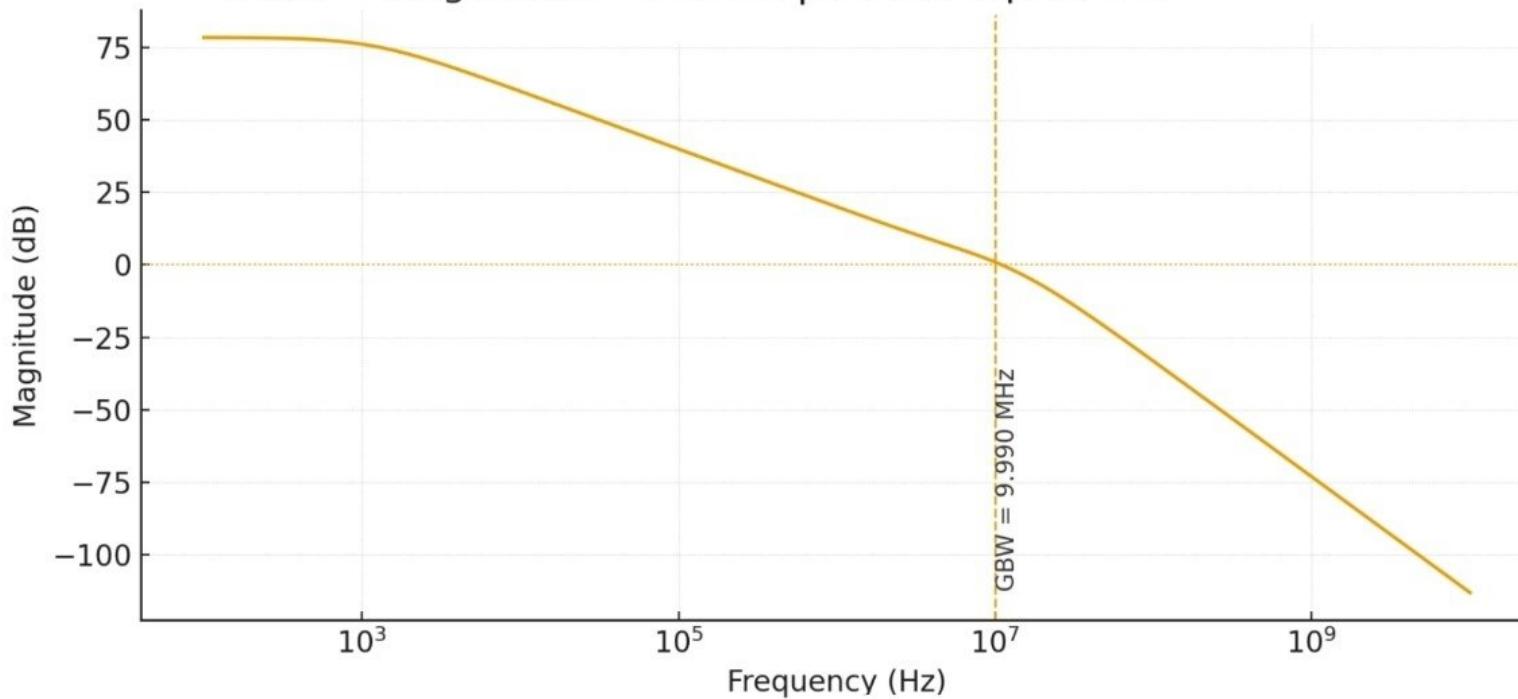Bode — Magnitude with compensated capacitor Cc



Bode — Phase

